

typical phase noise of -115 dBc/Hz @ 10 KHz MHz/V. Its industry standard MINI-16 package

offset and a typical tuning sensitivity of 9 is just 0.5 x 0.5 x 0.22"



power amplifier module for use in microwave radio, VSAT, military & space, fiber optic and broadband test equipment applications from 100 MHz to 20 GHz has been introduced. The HMC-C057 is a GaAs pHEMT MMIC PA in a miniature hermetic module



Coaxial to Waveguide Adapters Coaxial to Waveguide Adapters are offered in a variety of configurations. Option

A, broadband adapters, have excellent electrical specs that are maintained over the entire adapter bandwidth. Option B offers enhanced performance over a specific band of the unit's bandwidth



Digital Communication Analyzer The latest addition to the PXIT product

family, the PXIT 10G Digital Communication Analyzer (DCA) with Passive Optical Network (PON) filter rate options and smart

post processing for the PXIT N2100B DCA, helps optical transceiver test vendors reduce their cost of test.



LED Drivers This new family of LED driver ICs significantly reduces the number and size of external components required by drive circuits.

Operating at switching frequencies up to 600 kHz, AP880X Series step-down, DC-DC converters require only four smaller and lower cost inductors and/or capacitors.



RF Interface DAS Panel

Created to control the output power from PAs, the 15C2NB is designed to combine and attenuate RF

signals in steps of 1 dB up to 70 dB of maximum attenuation. With the operating frequency covering 800 MHz to 3 GHz, this design is ready for field deployment for GSM, PCS, WiMAX and LTE network architectures.



Phase-Locked **Crystal Oscillator** The PLXO-50 Phase-Locked Crystal Oscillator is used as the frequency reference in a surveillance RADAR

application. The PLXO, which operates at 50 MHz, maximizes system performance with its exceptional phase noise (<-150 dBc/Hz @ 10 KHz) and other features.



Directional Antenna A wide angle 2.4 GHz antenna, model HG2405P-135, is designed for compact installations and is

ideal for Wi-Fi, PCS, DCS, and custom applications. It gives the system designer wide angle coverage of an area without multiple antennas or larger footprint antennas



Band Reject Filters -Tunable Band stop and cavity filters that can be re-

3.	File	Edit	Parts	Set	Filter	Analyze	Yiew	Auto	Layout	Help	_ /# X
					Lum	ped Elemen	nt ential				
					Dist	ributed (Si	ngle-en	ided)			-
					Dist	ributed (Di	fferent	ial)			



Teories Deserves I ton	al mart		
Transmission Response Compass C Highpass C Bandpass C Bassel C Bassel C Bassel	Filter Specifications Cutoff Frequency Attenuation at Cutoff Passband Ripple Filter Drder Source Impedance	ut Other 5000 3.0103 0.150 7 50	MHz dB dB Ohms
		1 200	

All of the above produce more and more pronounced effects on circuit behavior as the operating frequency increases. Eventually, operation of the physical circuit will no longer resemble the circuit simulation if these circuit and component attributes are not accounted for. Fortunately, the LINC2 circuit design and simulation software from ACS (Escondido, CA) can accurately deal with all these issues.

To address the concerns of item 1, above, LINC2 has an extensive device library and enhanced physical component models to accurately model parasitic elements. Circuit elements in the LINC2 Parts menu are available to model the effects of item 2, while EM simulation can be used to simulate the effects of 3, 4 and 5.

This article will use the LINC2 filter synthesis software to design a lowpass distributed filter in microstrip to demonstrate the effects of transmission line discontinuities and other non-ideal elements on circuit performance. It will then be shown how EM simulation can be used to analyze the resulting performance shift and to determine how to correct for it.

adjusted by the

customer to new center frequencies are now available. These filters are tunable over a +/- 7.5% center frequency range with minimal change in bandwidth. Operating temperature range is -55 to +85°C.



Fast Rise/Fall Time

Logic Four new logic devices which are optimized for systems requiring fast rise/fall times, low

jitter, and low DC power consumption have been released. They provide operating clock and data rates of 13 GHz/13 Gbps, and are ideal for deployment in ATE, broadband T&M equipment, frequency synthesis and radar signal processing systems.



Ultra Low Phase Noise VCO Model CR01220A-LF in L-band operates at 1220 MHz with a tuning voltage range of 0 to 5 Vdc. This VCO features

a typical phase noise of -118 dBc/Hz @ 10 KHz offset and a typical tuning sensitivity of 2 MHz/V. It is well suited for satellite communication and microwave radio applications.



Design Verification Test Systems The GS-9000 Assisted GPS (A-GPS) Design Verification Test systems were designed around the 8960

wireless communications test set's new A-GPS assistance data messaging test capabilities. The capabilities support A-GPS validation, Total Isotropic Sensitivity testing and A-GPS pre-conformance testing for mobile devices.

Topology	Parametere Lauout	Other	1	
ropology	raidineters Layout	Guildi		
Add	itional Specifications -		-	
			~	
9	Series Element First, I	Minimum	Capacitor	
•	Shunt Element First, M	Ainimum	Inductor	
T	Line, Resonator Imped	lance:	50	Ohms
	T1			
	I Line, Minimum Imped	lance:	10	Unms
	TLine, Maximum Imped	lance:	90	Ohms
		istration la		
S	ynthesize Filter	EXIT	1	CANCEL

The LINC2 Filter program has a built-in interface to Sonnet's EM simulation software. The latest version of Sonnet® Lite™ is included free with LINC2 Pro (or can be downloaded free from Sonnet Software's web site at www.Sonnetsoftware.com/lite). The LINC2 Sonnet interface automatically starts the Sonnet EM program, sets up the EM simulation environment and exports the layout geometry into the Sonnet geometry editor (xgeom) ready for simulation.

ACS chose Sonnet Software as its first choice for integration into its LINC2 circuit simulation program because of Sonnet's outstanding overall performance, unrivaled accuracy and speed. Sonnet also has an excellent user interface that is easy to navigate. The Sonnet pop-up Quick Start Guide takes you through the process of setting up an EM simulation project from the beginning, including setting up the simulation environment, adding the geometry, analyzing and viewing the project results– all in wizard-like fashion! When using Sonnet with LINC2, this process is completed automatically. From LINC2, the entire design, geometry, and EM project setup is automatically transferred to Sonnet with a single menu click.



Distributed Microstrip Low-Pass Filter Design Example

For this example, the design specifications will include the following:

- Filter implementation: Low-pass stepped impedance microstrip filter
- Filter type: 7th order Chebyshev
- Material: Rogers RO4003[™]
- 3 dB cutoff frequency: 5000 MHz
- Stop-band attenuation at 7500 MHz: 35 dB
- Operating pass-band: 2500 4500 MHz
- Minimum microstrip impedance: 10 ohms
- Maximum microstrip impedance: 90 ohms
- Pass-band return loss: > 10 dB
- Pass-band ripple: 0.15 dB

The LINC2 filter synthesis program is started by selecting Filter Design from the LINC2 Tools menu as shown in **Figure 1**. This action opens the LINC2 Filter Synthesis Schematic Window, shown in **Figure 2**. LINC2 can design single-ended filters as well as differential filters for operation between balanced ports. For this example, Distributed (Single-ended) is selected from the Filter menu (**Figure 2**).

3. Part Parameters		Help -	F1	×
Reference Designator:	MS1		Tune	?
Dielectric Constant, Er:	3.38		Г	
Substrate Loss Tan, LT:	.0021		Г	
Metal Resistivity, Rho:	.7118	Gold=1	Г	
Metal Thickness, T:	.7		Г	
Metal Roughness, R:	.0125		Г	
Units Factor, U:	.0254	mm=1	Г	
Substrate Height, H:	8		Г	
Comment:	R4003			
From File				
Save File	ОК			
Figure 6: Microstrip Filte	r Substrate Par	ameters		

When the Design Specifications Form pops up, the design parameters for a 7th order low-pass Chebyshev filter are entered as shown in **Figure 3**.

The LINC2 Design Specifications Form is tailored to the type of filter selected, so the number and content of form tabs will vary somewhat from filter to filter. If there are layout-related issues to deal with, they will be listed by selecting the Layout tab. For the distributed lowpass Chebyshev filter selected here, there are no layout issues at this time.

The last tab, shown in **Figure 4**, lists the other miscellaneous details of the filter design specifications. On the Other form, the first element is specified as a shunt element. The minimum and maximum T-Line impedance is specified as 10 and 90 ohms respectively. At this point, clicking the Synthesize Filter button (**Figure 4**) generates the filter schematic shown in **Figure 5**.



Clicking Analyze now would yield simulation results for the schematic shown in **Figure 5** with ideal electrical transmission line components. The simulation results thus rendered on graphs and Smith chart displays of S21, S11 and S22 give a quick indication whether the final design is likely to meet specifications.

The next step is to use the Convert T-Lines to | Microstrip feature from the Auto menu. This action automatically converts all the ideal transmission line elements on the schematic page to physical microstrip based on a pop-up substrate definition form, as shown in **Figure 6**. The resulting converted schematic is shown in **Figure 7**. All of the physical dimensions required to build the filter are now contained on the schematic, including a description of the circuit board material. Anyone who has used a transmission line calculator to go through a schematic and manually convert all of the electrical (modeled) transmission lines to physical lines will appreciate the way LINC2 automates this process.



Clicking Layout produces the layout view shown in **Figure 8**. The length of de-embedding from the sides of the EM box is set to 50 mils. The EM box is the space over which the EM simulation will be performed. Simply clicking EM Simulation (Sonnet) pops up the Sonnet geometry editor (xgeom) with the LINC2 filter geometry already loaded.

View | View 3D now displays the filter geometry in three dimensions, as shown in **Figure 9**. The only action that is needed to get EM simulation results for the entire filter is to select Analyze from the Sonnet project editor; the software is really that easy to use!

When the EM simulation is completed, selecting Projects | View Response | New Graph displays the filter response plots on the graph shown in **Figure 10**. The heavy curves show the initial filter response before adjustment for the discontinuity effects of the large impedance steps between the shunt and series elements. The result is that the -3 dB cutoff frequency has shifted down by nearly 10% to 4540 MHz. This should not be surprising since the lumped circuit theory model for the step discontinuity is itself a lowpass structure with series inductance and shunt capacitance that acts to lower the cutoff frequency.



Both LINC2 and LINC2 Filter Pro have built-it Parts menus that include microstrip and stripline stepped width/impedance models for modeling these discontinuities. When the steppedimpedance lowpass filter in this example is simulated in LINC2 with these circuit theory discontinuity models added, the result is also a downward shift in the frequency response. With discontinuity modeling applied, the LINC2 simulation predicts a downward shift in the -3 dB cutoff frequency of about 8% to 4612.5 MHz.

The difference between Sonnet EM and LINC2 simulations is only 2% at 5GHz with this particular circuit and geometric structure. Circuit simulations of other structures may depend much more on EM simulation for accurate results. Also, as the operating frequency increases, EM simulation will almost always be needed to close the gap between simulated and measured performance.

Improved Synthesis Using EM Analysis

The EM simulation indicated that the effect of the stepped-impedance microstrip discontinuities was a downward shift of 460 MHz in the cutoff frequency. In less than a minute, another filter synthesis run can be completed, this time compensating for the frequency shift by specifying a cutoff frequency of exactly 460 MHz higher (or Fc = 5460 MHz). This was done and the results from the new EM simulation are shown as the light colored plots overlaid the original (heavy plots) in **Figure 10**. The new -3 dB cutoff frequency is now 5.02 GHz. This reduced the error in cutoff frequency from 10% to 0.4% in one iteration. All of the other original filter goals have been met, including return loss and stop-band attenuation.



Summary and Conclusions

This stepped-impedance lowpass filter design was used to show how EM simulation can be used to uncover the effects of transmission line discontinuities in distributed filters, thus improving the accuracy of the simulation. As was shown in this example, lumped (circuit theory) discontinuity models can be included in the schematic based simulation to improve the accuracy. However, these transition models are usually based on lumped LC approximations. This means that there is a limit on the size of the discontinuity, the substrate dielectric, and in many cases, there are limitations on the frequency range as well.

In this example, the ratio of the line widths at the impedance steps was nearly 28. The schematic based line width/impedance step models typically are only accurate to within a few percent for steps less than 10:1. Since these kinds of filters have such large impedance steps, it is a good idea to use EM simulation for the best results.

LINC2 is a high performance RF and microwave design and simulation program from ACS. In addition to schematic based circuit simulation, optimization and statistical yield analysis, LINC2 Pro includes many value-added features for automating design tasks, including circuit synthesis. LINC2 directly interfaces to leading RF and microwave design suites, allowing it to be used standalone or by leveraging its capabilities with those of other major packages. The subject of this article, the LINC2 Sonnet interface, uses a single button click to automatically transfer the LINC2 layout geometry into Sonnet for world-class EM analysis. More information about LINC2 can be

found on the ACS web site at www.appliedmicrowave.com.

Sonnet is a trademark of Sonnet Software, Inc. All trademarks and registered trademarks are the property of their respective owners.

Applied Computational Sciences http://www.txtlinx.com/txtsys/advercountin.asp?adverid=558&prodid=100 TXTLINX.COM 100 Email this article to a friend!

Copyright © 2007 Octagon Communication Inc. DBA MPDigest / MPDigest.com, All Rights Reserved.